

# Foresight's Fantastical Circuit Lab: The Great Conductivity Challenge!

---

## Materials Needed

- One (1) 9-volt battery
  - One (1) 9-volt battery snap connector with wire leads
  - One (1) low-voltage LED light (any color)
  - Three (3) insulated wires with alligator clips on both ends
  - **Testing Materials:** A collection of small, safe household items. Suggestions:
    - Metal: paperclip, aluminum foil, key, coin, spoon
    - Non-Metal: plastic ruler, rubber eraser, wooden craft stick, piece of cotton fabric, glass marble, ceramic mug
    - "Mystery Items": a graphite pencil (test the wood and the graphite tip separately!), a cup of tap water, a cup of salt water, a cup of sugar water
  - A notebook or piece of paper (for the "Lab Report") and a pencil
- 

## Lesson Plan Details

### 1. Learning Objectives

By the end of this lesson, Foresight will be able to:

- **Design and Build:** Construct a simple, open circuit that functions as a conductivity tester.
- **Test and Classify:** Systematically test at least 10 different household materials and classify them as either electrical conductors or insulators based on experimental evidence.
- **Apply and Create:** Use the principles of conductivity to design and build a simple, functional electrical device, such as a game or an alarm.

### 2. Alignment with Standards and Curriculum (Middle School Physical Science)

- **MS-PS2-3:** Ask questions about data to determine the factors that affect the strength of electric and magnetic forces. (This lesson provides a foundational understanding of how materials allow electric current to flow.)
- **Engineering Design (MS-ETS1-1):** Define the criteria and constraints of a design problem with sufficient precision to ensure a successful solution. (This is addressed in the creative design challenge.)

### 3. Instructional Strategies & Lesson Activities

#### Part 1: The Hook - A Spark of Curiosity (5 minutes)

Let's start with a question, Foresight. Imagine you have two glasses of water that look identical. One is pure water, and the other is salt water. Without tasting them, how could you use electricity to figure out which is which? Today, we're going to build a special tool that can answer that question and many more! We're going to uncover the secret electrical properties hidden in everyday objects.

---

## Part 2: The Build - Creating the Conductivity Tester (10 minutes)

Our first mission is to build our scientific instrument. We will assemble it step-by-step. Remember, a circuit is just a complete circle or path for electricity to travel.

1. **Connect the Power:** Snap the battery connector onto the 9-volt battery. This is our power source.
2. **Add the Light:** An LED has two legs (leads), one slightly longer than the other. The **longer leg is positive (+)**.
  - Take the **red wire (+)** from the battery snap and connect it to the longer leg of the LED using an alligator clip.
3. **Start the Path Back:** Connect a second alligator clip wire to the **shorter leg (-)** of the LED. Let the other end of this wire hang free for now.
4. **Complete the Tester:** The **black wire (-)** from the battery snap is also free. You now have two unattached alligator clips. These are your testing probes! When these two clips touch a material that conducts electricity, they will complete the circuit and the LED will light up.

**Safety Check:** Touch the two free alligator clips together. The LED should light up brightly. This confirms your circuit works! Now, let's keep them apart and move on to the experiment.

## Part 3: The Experiment - The Great Conductivity Challenge (15-20 minutes)

It's time to become a materials scientist! Grab your notebook and create a "Lab Report" chart with three columns: **Material Name**, **My Prediction (Conductor or Insulator?)**, and **Result (Light On or Off?)**.

1. Go on a scavenger hunt for the testing materials listed above (or any others you find interesting!).
2. For each item, write its name in your chart and make a prediction. Do you think it will let electricity pass through it?
3. Test your prediction! Firmly touch the two alligator clip probes to the object, making sure the clips don't touch each other.
  - If the LED lights up, the material is a **CONDUCTOR**. Record this in your chart.
  - If the LED does not light up, the material is an **INSULATOR**. Record this in your chart.
4. Test all your items, including the "mystery items" like salt water and the pencil lead. What surprised you?

## Part 4: The Invention - The Creative Design Challenge (15 minutes)

Now that you're an expert on conductors and insulators, let's put that knowledge to work. Your challenge is to invent a simple device using your conductivity tester. Choose one of these ideas or invent your own!

- **The Steady Hand Game:** Use a long piece of conductive material (like a bent paperclip or a piece of wire from a coat hanger). Form another piece of wire into a loop with a handle. The challenge is to move the loop from one end of the bent wire to the other without them touching. If they touch, the LED lights up, and you lose!
- **The Rain Alarm:** Place two alligator clips very close together (but not touching) on a dry paper towel. What happens when you add a few drops of water? You've just invented a device that can tell you when it's raining!
- **The Quiz Buzzer:** Create two pads out of aluminum foil. Connect one alligator clip to each pad. When two players want to "buzz in" for a quiz, the first one to touch both pads with their hands completes the circuit and lights the LED. (Our bodies are conductors!)

## 4. Engagement and Motivation

This lesson is designed to feel like a lab investigation and an invention session, not a lecture. Foresight has the freedom to choose materials to test and an invention to build, giving him ownership over the learning process. The hands-on nature of building the circuit and the "Aha!" moment when the LED lights up are highly motivating.

## 5. Differentiation and Inclusivity

- **To Increase the Challenge:** Introduce the concept of **resistance**. Ask: "Why does the LED seem dimmer when you test the pencil lead compared to the paperclip?" This leads to a discussion that not all conductors are equal. You can even swap the LED for a buzzer to explore how sound might change.
- **To Provide Support:** If circuit building is tricky, pre-assemble the battery, LED, and one wire, leaving only the final two probes to be connected. Focus more on the discovery and classification part of the activity.

## 6. Assessment Methods

- **Formative (During the lesson):** Observe Foresight as he builds the circuit and tests materials. Ask questions like, "Why do you predict that will be an insulator?" or "What do all the conductors seem to have in common?"
- **Summative (End of lesson):**
  1. **Lab Report Review:** Discuss the results of his conductivity chart. Were there any surprises?
  2. **Invention Demonstration:** Foresight presents his creative invention and explains *why* it works using the key vocabulary words: **conductor**, **insulator**, and **complete circuit**.

## 7. Organization and Clarity

The lesson flows logically from introduction to hands-on building, guided experimentation, and creative application. Each part builds on the last, ensuring concepts are understood before moving to a more complex task. Clear, numbered steps and bolded keywords make the instructions easy to follow.

## 8. Creativity and Innovation

Instead of memorizing definitions, Foresight discovers the concepts of conductivity and insulation through his own experimentation. The final part of the lesson is purely creative, tasking him with moving from a scientist (discovering principles) to an engineer (applying principles to solve a problem or create something new).

## 9. Materials and Resource Management

The materials are common, relatively inexpensive, and easily sourced from a local electronics store or online. The use of everyday household items for testing makes the lesson accessible and reduces preparation time. The core "tester" can be saved and used for future electronics projects.

**IMPORTANT SAFETY NOTE:** We are only using a low-voltage battery. This is very safe. However, it is critical to always remember this rule: **NEVER, EVER experiment with electricity from a wall outlet.** It is extremely dangerous and can cause serious injury.